



**END SEMESTER ASSESSMENT (ESA)  
B.TECH. (CSE)  
III SEMESTER**

**UE22CS251A – DIGITAL DESIGN & COMPUTER  
ORGANIZATION LABORATORY**

**PROJECT REPORT**

**ON**

**3 BIT UP/DOWN COUNTER**

**SUBMITTED BY**

**NAME**

**SRN**

**1) Shreya S**

**PES2UG22CS534**

**2) Shashank Bakshi**

**PES2UG22CS518**

**3) Shreya Madhusudan**

**PES2UG22CS533**

**AUGUST – DECEMBER 2023**

**DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING**

**ELECTRONIC CITY CAMPUS,**

**BENGALURU – 560100, KARNATAKA, INDIA**

TABLE OF CONTENTS		
Sl.No	TOPIC	PAGE No
1.	ABSTRACT OF THE PROJECT	
2.	CIRCUIT DIAGRAM	
3.	MAIN VERILOG CODE	
4.	TEST BENCH FILE	
5.	SCREEN SHOTS OF THE OUTPUT	

# ABSTRACT OF THE PROJECT:

## Abstract:

This project focuses on the design and implementation of a 3-bit up/down ring counter using the Verilog hardware description language. A ring counter is a type of digital counter that cycles through a sequence of states in a circular manner. The counter developed in this project is capable of counting both upwards and downwards, providing versatility in its applications.

The primary objective of this project is to create a 3-bit ring counter that counts upwards and downwards based on user-defined conditions. The implementation involves the use of Verilog to describe the counter's behavior, including the definition of finite states through a Finite State Machine (FSM).

The project employs a systematic approach to design, beginning with the definition of the counter's states and transitions using an FSM. The Verilog hardware description language is then utilized to translate the FSM into synthesizable code. The counter's functionality includes counting upwards in a sequential manner and counting downwards by decrementing from the highest state.

**Finite State Machine (FSM):** The states of the FSM represent the different values of the counter, and transitions between states are triggered by clock edges and user-defined conditions. By incorporating an FSM, the design ensures a clear, organized, and systematic approach to controlling the counter's operation.

### 1. States:

- In a 3-bit up/down counter, the states represent the different values the counter can hold. Since it's a 3-bit counter, it can represent values from 0 to 7 (binary 000 to 111).
- So, there are eight possible states: 000, 001, 010, 011, 100, 101, 110, 111.


### 2. Inputs:

- The inputs to the FSM are the signals that control the counter's behaviour. In this case, there are typically two inputs:
  - **Count Up (CU):** This input signal increments the counter by 1.
  - **Count Down (CD):** This input signal decrements the counter by 1.


### 3. Transitions:

- The transitions between states are determined by the inputs. For example:
  - If the current state is 010 and CU is asserted, the next state will be 011.
  - If the current state is 101 and CD is asserted, the next state will be 100.

## FSM DIAGRAM

 

## CIRCUIT DIAGRAM:

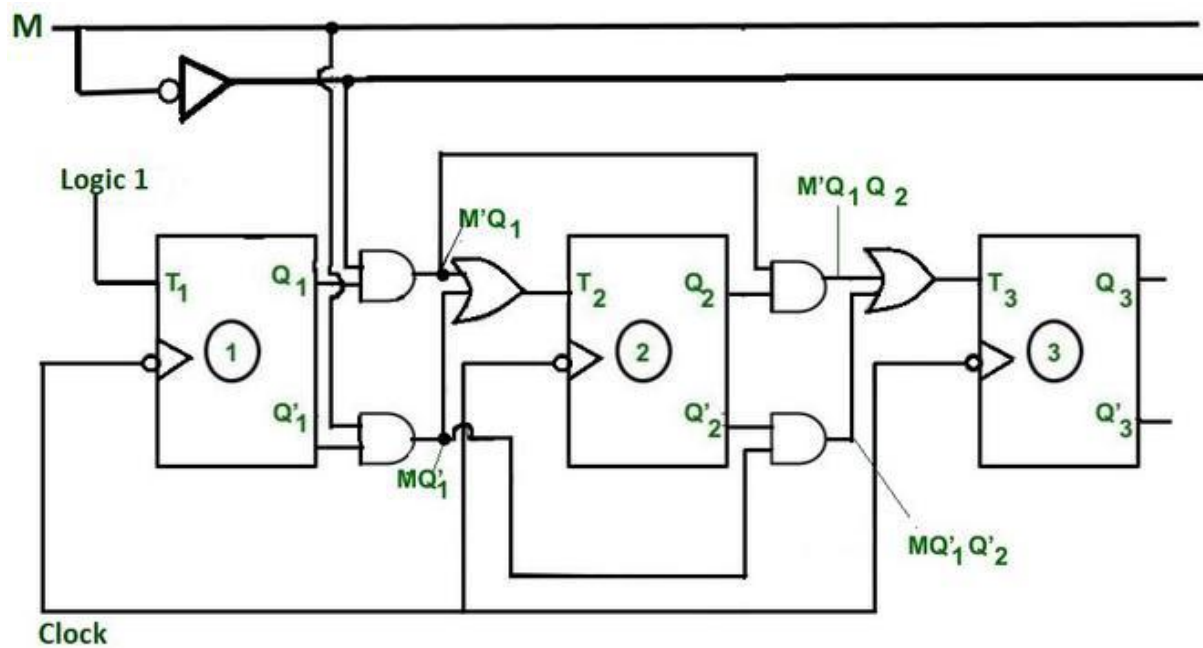

# MAIN VERILOG CODE:

```
module up_counter(input clk, reset, output[3:0] counter);

    reg [3:0] counter_up;                // Initialise register counter_up to find up
    counter states                       // counter states

    always @(posedge clk or posedge reset) // Postive edge triggered circuit
    begin
        if(reset)
            begin
                counter_up = 4'd0;        // If reset==1, set counter to 0000
            end
        else
            begin
                counter_up = counter_up + 4'd1; // Else, add 0001 to counter
            end
        end
        assign counter = counter_up;      // Return new value of counter
    endmodule
```

```
module down_counter(input clk, reset, output [3:0] counter);

    reg [3:0] counter_down;             // Initialise register counter_down to find
    down counter states                 // counter states

    always @(posedge clk or posedge reset) // Postive edge triggered circuit
    begin
        if(reset)
            begin
                counter_down = 4'hf;      // If reset==1, set counter to 1111
            end
        else
            begin
                counter_down = counter_down - 4'd1; // Else, subtract 0001 from counter
            end
        end
        assign counter = counter_down;    // Return new value of counter
    endmodule
```

## TEST BENCH FILE:

```
module counter_testbench();
    reg clk, reset;
    wire [3:0] counter1,counter2;

    up_counter up(clk, reset, counter1);
    down_counter down(clk, reset, counter2);

    initial begin
        $dumpfile("Counter.vcd");
        $dumpvars(0,counter_testbench);
    end
    initial begin
        clk=0;
        repeat(96)
            #5 clk=~clk;
    end
    initial begin
        reset = 1;
        #10
        reset = 0;
    end
end
endmodule
```

# SCREEN SHOT OF THE OUTPUT:

